



Micro Processor Project


# **Angry Tanks**

by

**Abdallah Mohamed Nasser - 7103755**


this document is licensed under (GFDL) GNU Free Documentation License

## Hardware Diagram :

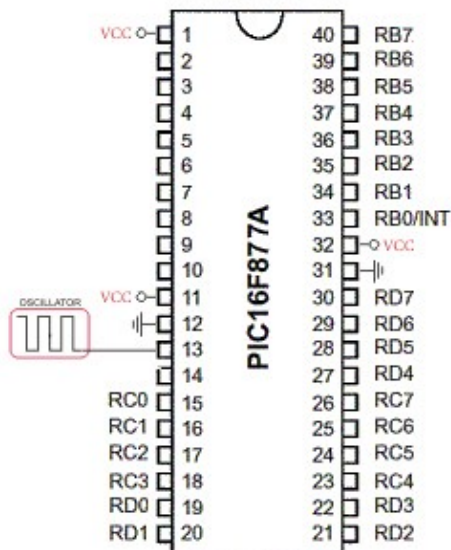

RB0 <> (S0 or s1 or s2 or s3)  
 RB1 <> CS1  
 RB2 <> CS2  
 RB3 <> RS  
 RB4 <> R/W  
 RB5 <> EN  
 RB6 <> RST  
 RB2 <> CS2

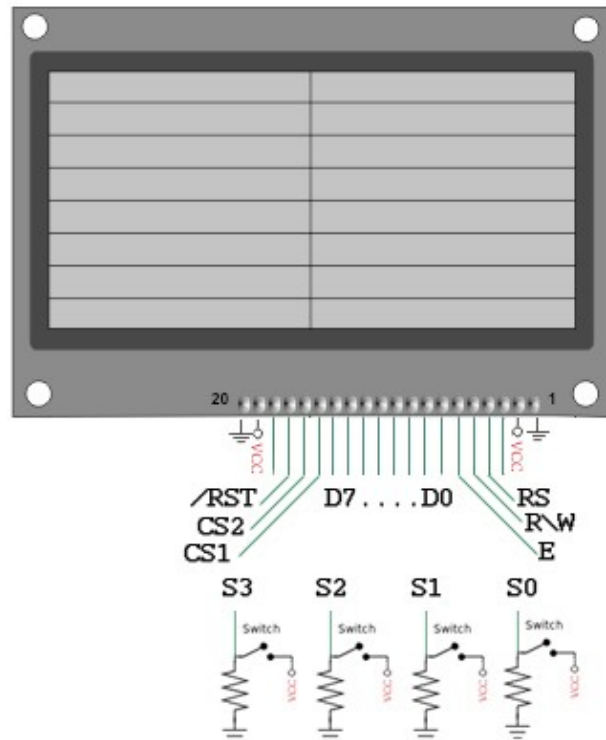RC0 - RC7 <> D0 - D7  
 RD0 - RD3 <> S0 - S3



## Hardware Used :

- PIC 16f877a
- GLCD (LM12864LFW )
- 4 Push Buttons
- LEDs for testing